

Activity 1

Activity 1

#1

(R)esistor	Measured	Expected	% Error
R1	326	330	1.21212121212121
R2	985	1000	1.5
R3	10020	10000	0.2
R4	21600	22000	1.81818181818182

#2

(R)esistor

R1	R2	R3	R4	Resistance	Expected
326	985	0	0	1330	1311
326	985	10020	21600	33000	32931

Activity 1

% Error

1.44927536231884

0.209529015213629

Activity 2

Activity 2

#1

(R)esistor	Measured	Expected	% Error
R1	217	220	1.36363636363636
R2	324	330	1.81818181818182
R3	557	560	0.535714285714286
R4	985	1000	1.5

#2

(R)esistor	Measured	Voltage	Current	expected current	% difference
R1	217	6	27.2	27.6497695852535	1.62666666666668
R2	324	6	18.3	18.5185185185185	1.18
R3	557	6	10.6	10.7719928186715	1.59666666666668
R4	985	6	6	6.09137055837563	1.49999999999999

#3

Broken	Current	Voltage	Resistance
R1	6	6	10000
R2	6	6	10000
R3	3.9	6	1538461.53846154
R4	2.5	6	2400000